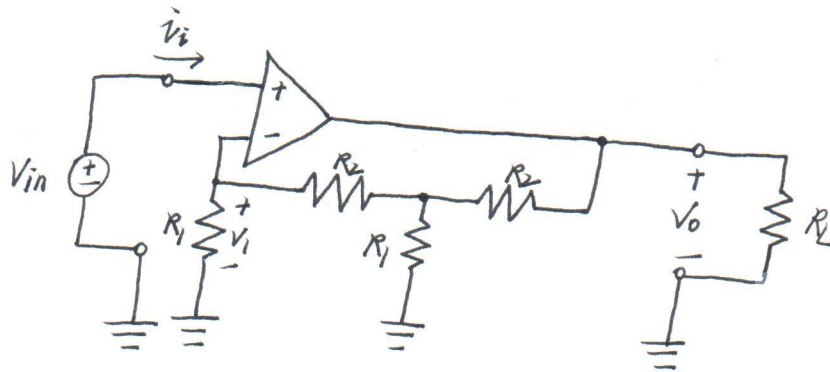


4.6



First, we verify that negative feedback is present


(a)

According to the summing-point constraint:

$$i_i = 0$$

$$V_{in} = V_i$$

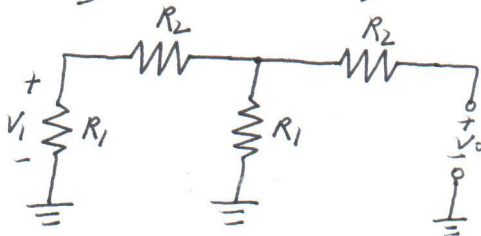According to the voltage-divider principle:



$$V_{in} = V_i = V_o \frac{R_1^2}{R_1^2 + 3R_1R_2 + R_2^2}$$

$$A_v = \frac{V_o}{V_{in}} = 1 + \left(\frac{R_2}{R_1}\right)^2 + 3\left(\frac{R_2}{R_1}\right)$$

(b)

For $R_1 = 1k\Omega$ and $R_2 = 10k\Omega$

$$A_v = 131$$

(c)

$$R_{in} = \frac{V_{in}}{i_i} = \infty \text{ (theoretically)}$$

(d)

$$R_o = 0\Omega$$