
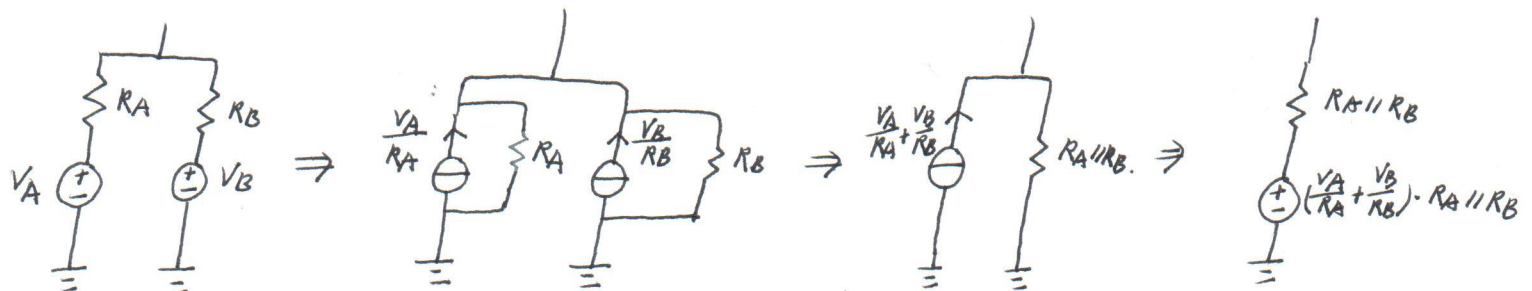


# Chapter 4

4.1

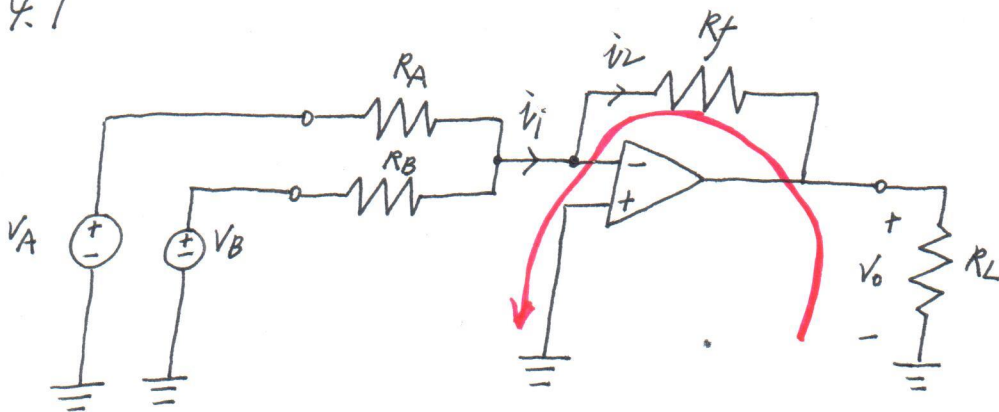

(a) First, we verify that negative feedback is present  
According to the summing-point constraint:

$$i_1 = \left( \frac{V_A}{R_A} + \frac{V_B}{R_B} \right) \cdot R_A || R_B \div (R_A || R_B) = \frac{V_A}{R_A} + \frac{V_B}{R_B}$$

$$i_2 = i_1 = \frac{V_A}{R_A} + \frac{V_B}{R_B}$$

Writing a voltage equation around the loop that includes the output terminal, the resistor  $R_f$ , and op-amp input terminal:

$$V_o + i_2 R_f = 0$$

$$\therefore V_o + \left( \frac{V_A}{R_A} + \frac{V_B}{R_B} \right) R_f = 0$$

$$V_o = - \left( \frac{R_f}{R_A} \right) V_A - \left( \frac{R_f}{R_B} \right) V_B$$

(b) The input resistance for  $V_A$  is equal to  $R_A$ .

(c) The input resistance for  $V_B$  is equal to  $R_B$ .

(d) The output resistance is zero.